

Dept. of CSE, Bennett University
ECSE108L - Digital Design
Lab Assignment - 06

Q 1. A half-adder is used to add two single bit inputs. It produces a single bit output and a possible carry bit. Below is the truth table for the same.

Input		Output	
A	B	Carry	Output
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


- (i) Develop the Boolean expression and logic circuit for the given truth table.
- (ii) Write a Verilog module for Universal NOR gate. Utilize the **instances of NOR gate** only to write a structural Verilog code for Half adder.
- (iii) Verify it with respective testbench code.

Q 2. The half adder in the previous question can only add two one bit numbers when there is no carry bit, which is not sufficient in many cases. While a full-adder has two one-bit inputs, a carry-in input, a sum output, and a carry-out output. Below truth table represents a full-adder.

Full Adder Truth Table				
Input			Output	
A	B	Cin	Cout	Sum
0	0	0	0	0
1	0	0	0	1
0	1	0	0	1
1	1	0	1	0
0	0	1	0	1
1	0	1	1	0
0	1	1	1	0
1	1	1	1	1

- (i) Utilize the above truth table to design the Boolean expression and digital circuit for the full adder.
- (ii) Write the behavioral Verilog code for the full adder.
- (iii) Verify it with respective Testbench code.

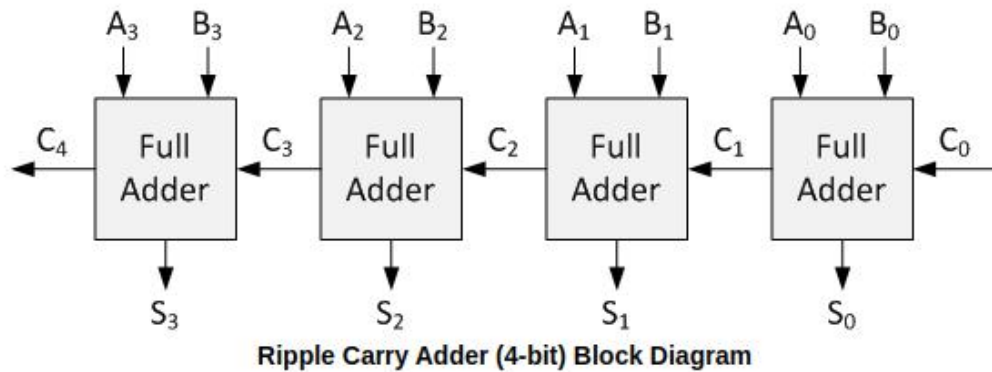Q 3. The full adder designed in previous question is able to add only two one bit inputs. We can advance our design by adding N number of full adders to create a N bit Ripple carry adder. A block diagram for 4-bit Ripple carry adder can be expressed as:



- (i) By using the instances of full adder module created in Question 2, now create a 4-bit Ripple carry adder Verilog module.
- (ii) Write a Testbench code to verify it. (you may take 1101 and 1011 as input values)

Q 4. We can also utilize a adder module to perform the subtraction of binary numbers with the help of 2's complement. Use the Ripple adder module developed in previous question to develop a binary subtraction module.

Verify your code by a suitable Testbench code and test it for following inputs.

- (a) 1011 - 1001
- (b) 1010 - 1110

Note:

The syntax for multi-bit port declaration is as follows:

port_direction data_type [port_size] port_name

Example:

```
input [1:0] a_in // a two bit [1, 0] names a_in
output reg [2:0] b_in // a three bit register type output port named as b_in
```